

University of Victoria
Department of Computer Science
CSC 355 Digital Logic and Computer Design
ASSIGNMENT 1 DUE Thursday September 24 AT BEGINNING OF CLASS

Neatness Counts!

It is expected that answers to assignments are either typed or written *extremely* neatly. In all cases, the Karnaugh Maps formats below *must* be used, either copied and edited to add the required bits and circles or printed and written on.

1. Determine the radix r given that $(257)_r = (11010110)_2$ (show all your work).

$$(11010110)_2 = 128 + 64 + 16 + 4 + 2 = 214_{10}$$

Note: It is clear that r is less than 10 because 214 is smaller than 257.

Using a trial and error method, guess 9:

$$2 \times 9^2 + 5 \times 9 + 7 = 162 + 45 + 7 = 214_{10} \quad \therefore \text{base 9 is the correct answer!}$$

2. Simplify the following expression, using Boolean algebra, into minimum sum of products form:

$$(B + C)(\bar{B} + D)(\bar{A} + C)(\bar{A} + \bar{D})$$

Show each Boolean algebra rule used in the simplification.

$$\begin{aligned} (B + C)(\bar{B} + D)(\bar{A} + C)(\bar{A} + \bar{D}) &= (B\bar{B} + BD + \bar{B}C + CD)(\bar{A}\bar{A} + \bar{A}C + \bar{A}\bar{D} + C\bar{D}) && \text{, distributive} \\ &= (BD + \bar{B}C + CD)(\bar{A} + \bar{A}C + \bar{A}\bar{D} + C\bar{D}) && \text{, complement, idempotent} \\ &= (BD + \bar{B}C)(\bar{A} + C\bar{D}) && \text{, consensus, absorption} \\ &= \bar{A}BD + \bar{A}\bar{B}C + BCD\bar{D} + \bar{B}CC\bar{D} && \text{, distributive} \\ &= \bar{A}BD + \bar{A}\bar{B}C + \bar{B}C\bar{D} && \text{, complement, idempotent} \end{aligned}$$

3. Convert the following expression into minimum product of sums form :

$$\bar{A}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{D} + ACD + \bar{A}BD$$

$$F = \bar{A}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{D} + ACD + \bar{A}BD$$

		CD			
		00	01	11	10
AB	00	1	0	0	0
	01	1	1	1	0
	11	0	0	1	0
	10	1	0	1	1


$$F' = B'C'D + ABC' + A'B'C + BCD'$$

$$\therefore F = (B + C + D')(A' + B' + C)(A + B + C')(B' + C' + D)$$

4. Design circuits as specified below. In each case assume that all variables are available in both true and inverted form. Gates may have any fan-in up to 4. Marks will be awarded for keeping the total number of gates as small as possible.

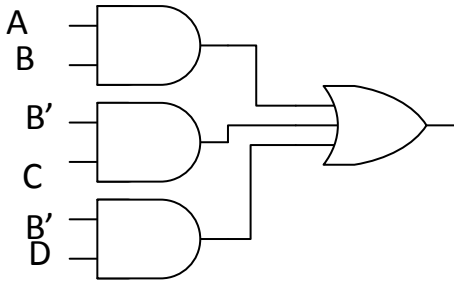- a. a two level circuit for $a(b + a') + b'(c + d) + ab$ using only AND, OR gates;

$F = a(b + a') + b'(c + d) + ab = ab + aa' + b'c + b'd + ab = ab + b'c + b'd$




Its already minimal. . . I did not need the K-map!

		CD			
		00	01	11	10
AB	00		1	1	1
	01				
	11	1	1	1	1
	10		1	1	1

- b. a circuit for $a'bc + a'b'd + a'c$ using NOR gates only


$F = a'bc + a'b'd + a'c$

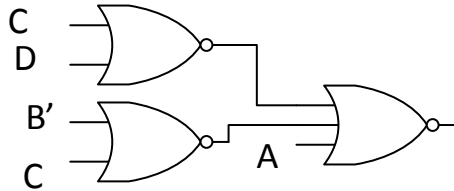

		CD			
		00	01	11	10
AB	00	0	1	1	1
	01	0	0	1	1
	11	0	0	0	0
	10	0	0	0	0


$F' = c'd' + bc' + a \quad \therefore F = (c+d)(b'+c)a'$

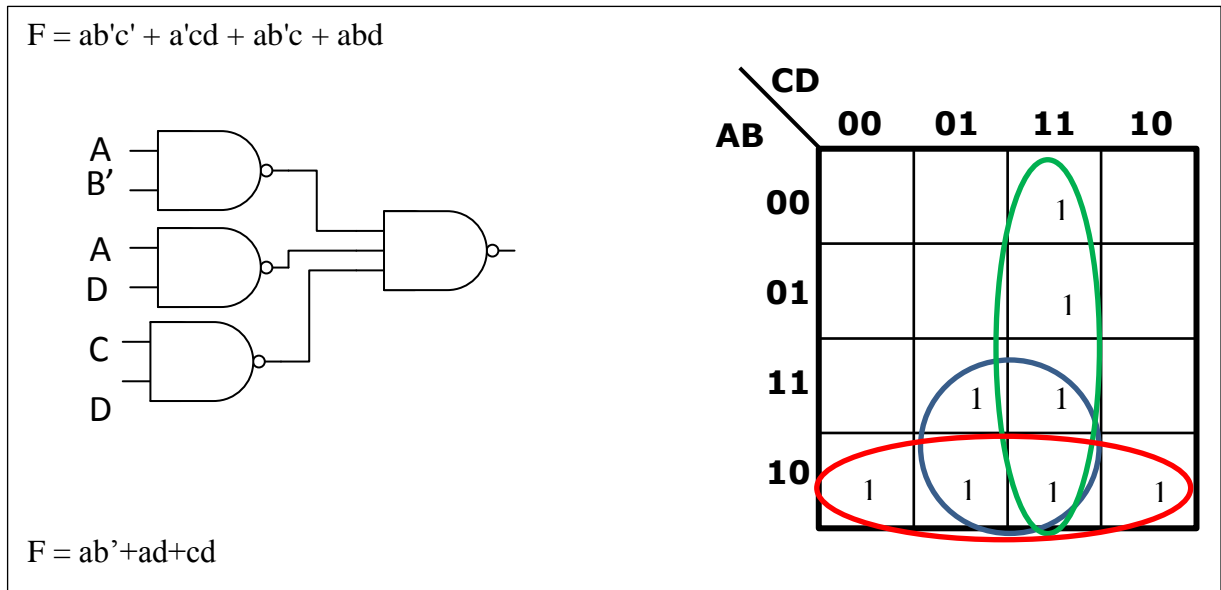- c. a circuit for $ab'c' + a'cd + ab'c + abd$ using NAND gates only.




5. Simplify the following Boolean expressions (to the simplest sum of products form) using three variable maps.

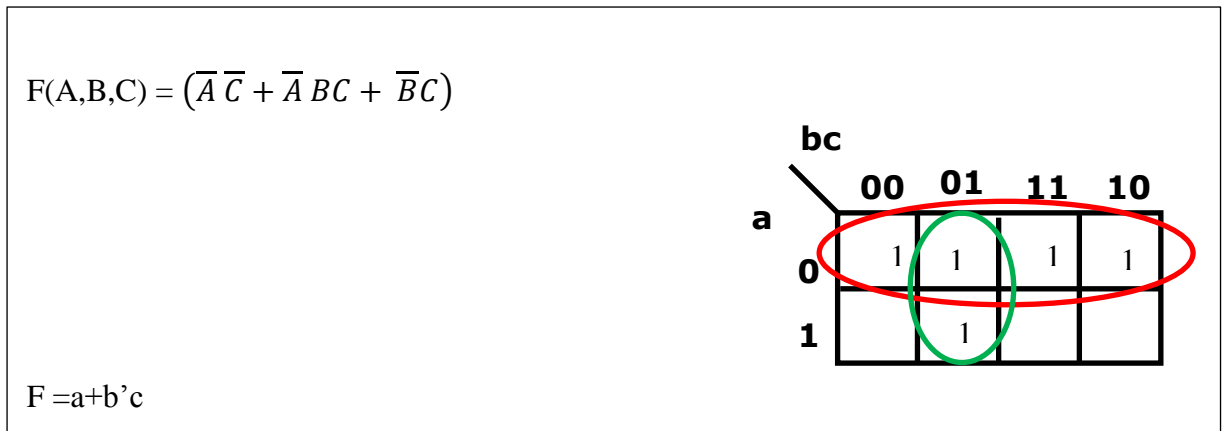a. $F(A,B,C) = (\overline{A} \overline{C} + \overline{A} BC + \overline{B} C)$




b. $F(X,Y,Z) = \sum m(0,2,6,7)$

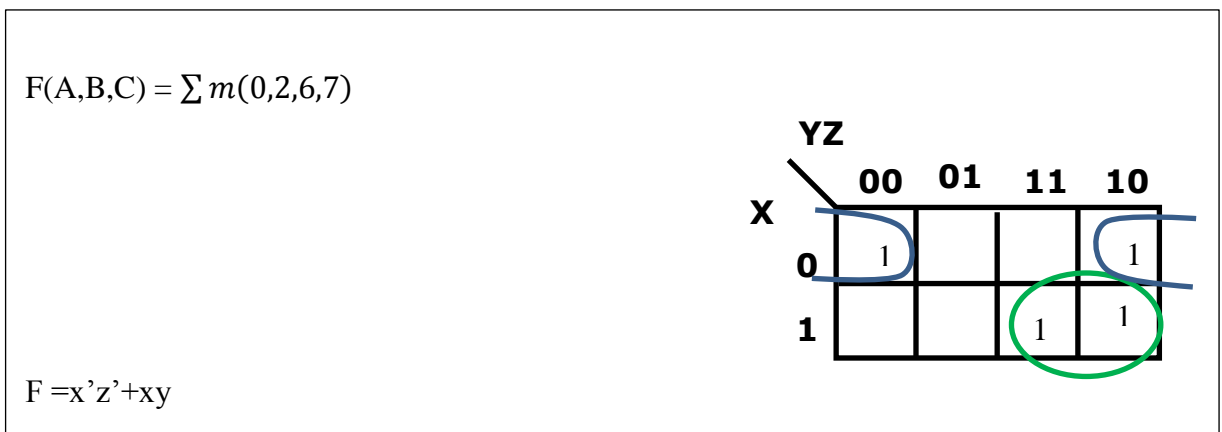

6. Simplify the following Boolean expressions (to the simplest sum of products form) using four variable maps:

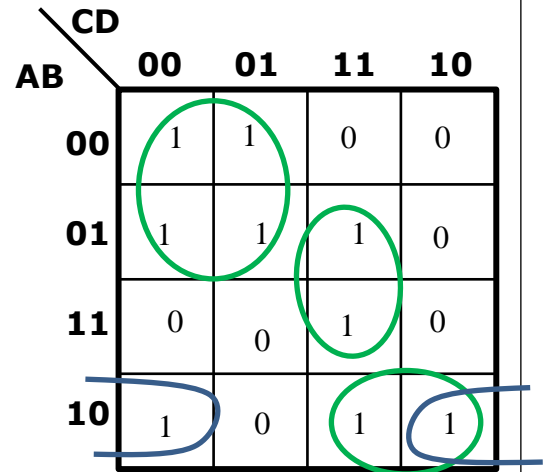a. $F(A,B,C,D) = (A + B + \overline{C})(\overline{A} + \overline{B} + D)(\overline{A} + C + \overline{D})(A + \overline{C} + D)$

$$F(A,B,C,D) = (A + B + \overline{C})(\overline{A} + \overline{B} + D)(\overline{A} + C + \overline{D})(A + \overline{C} + D)$$




$$F = A'C' + BCD + AB'D' + AB'C$$

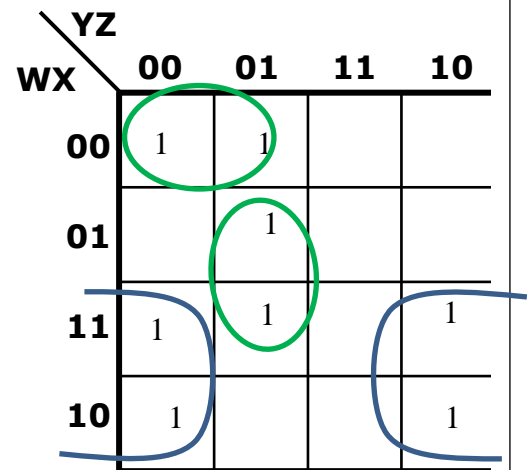b. $F(w,x,y,z) = \sum m(0, 1, 5, 8, 10, 12, 13, 14)$

(3 terms)

$$F(A,B,C,D) = \sum m(0, 1, 5, 8, 10, 12, 13, 14)$$




$$F = W'X'Y' + XY'Z + WZ'$$

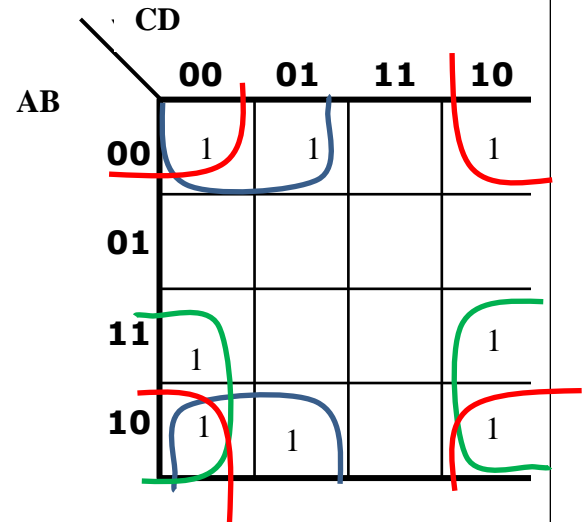c. $F(w,x,y,z) = \sum m(0, 1, 2, 8, 9, 10, 12, 14)$

(3 terms)


$F(A,B,C,D) = \sum m(0, 1, 2, 8, 9, 10, 12, 14)$



7. Given the function $F(w,x,y,z) = \sum m(1, 3, 7, 13) + d(4, 5, 9, 14)$. Find:

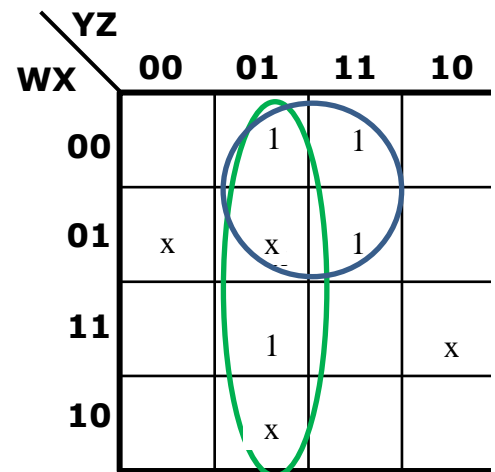a. the minimum sum of products form for F

$F(w,x,y,z) = \sum m(1, 3, 7, 13) + d(4, 5, 9, 14)$



- b. the minimum product of sums form for F.

$$F(w,x,y,z) = \sum m(1, 3, 7, 13) + d(4, 5, 9, 14).$$

YZ WX	00	01	11	10
00	0	1	1	0
01	x	x	1	0
11	0	1	0	x
10	0	x	0	0

$$F' = Z' + WY \quad \therefore F = Z(W' + Y')$$

8. A switching network has 3 inputs and 2 outputs. The output variables, a and b, represent the first and second bits, respectively of a binary number, N. N equals the number of inputs which are “1”. For example, if w=1, x=0, y=1, then a=1, b=0.
- Find the minterm expansion for a and b.
 - Find the maxterm expansion for a and for b.

Express each answer in abbreviated notation (with Σ or Π).

w	x	y	a	b
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

- $a = \Sigma m(3, 5, 6, 7)$
 $b = \Sigma m(1, 2, 4, 7)$
- $a = \Pi M(0, 1, 2, 4)$
 $b = \Pi M(0, 3, 5, 6)$