

1. The SOP of :  $F(A,B,C,D) = \sum m(1,2,3,5,6,9) + \sum d(7,10,11,12,13)$

AB\CD	00	01	11	10
00				
01				
11				
10				

2. The circuit that represents the SOP of  $F(A,B,C,D)$  using OR gates, AND gates and inverters (on main inputs).

3. The POS of :  $F(A,B,C,D) = \sum m(1,2,3,5,6,9) + \sum d(7,10,11,12,13)$

AB\CD	00	01	11	10
00				
01				
11				
10				

4. Draw the POS form of the circuit using OR and AND gates (plus inverters on the main inputs.)

5. Re-draw the circuit using only 2-input NOR gates (plus inverters on the main inputs.) Include pin numbers.

6. Karnaugh maps and simplified functions  $X$ ,  $Y$ , and  $Z$

$A \backslash BC$		00	01	11	10
0	0				
	1				

$X$

$A \backslash BC$		00	01	11	10
0	0				
	1				

$Y$

$A \backslash BC$		00	01	11	10
0	0				
	1				

$Z$

7. Draw circuits for  $X$ ,  $Y$ , and  $Z$  using only 2-input NAND gates and Inverters on the inputs. Include chip pin numbers on all inputs and outputs.

Finally, write a list of things that you learned in doing this pre-lab: