

2. Truth table:

3. Karnaugh Map:

		00	01	11	10
00					
01					
11					
10					

5&6. Your Circuit: (Please be neat & indicate pin numbers on all chips.)

Strobe is connected to: _____

8. Truth Table:

9.

A\BC	00	01	11	10
0				
1				

A\BC	00	01	11	10
0				
1				

10. Your Circuit: (Please be neat & indicate pin numbers on all chips.)