

University of Victoria
Department of Computer Science
CSC 355 Digital Logic and Computer Design

ASSIGNMENT 3

SHOULD BE DUE: Thursday November 12 AT BEGINNING OF CLASS
BUT WILL BE ACCEPTED UNTIL: Thursday December 3 AT BEGINNING OF CLASS

Neatness Counts!


1. Given the next state and output table shown below, give an implementation of the clocked sequential machine using 3 RS flip-flops (labeled A, B and C) plus any other gates you require, based on the state assignment $S_0 = 001$, $S_1 = 000$, $S_2 = 100$, $S_3 = 110$, $S_4 = 010$, $S_5 = 111$, $S_6 = 011$. Make the best use of don't cares. Show:
- A state diagram.
 - The next state maps for each flip-flop and the output map
 - The maps for each of the six flip flop input equations that are required.
 - The minimized logic functions derived from above.

state	Next state		Output	
	x = 0	x = 1	x = 0	x = 1
$S_0 001$	$S_1 = 000$	$S_2 = 100$	1	1
$S_1 000$	$S_3 = 110$	$S_4 = 010$	1	0
$S_2 100$	$S_1 = 000$	$S_4 = 010$	1	1
$S_3 110$	$S_5 = 111$	$S_2 = 100$	1	0
$S_4 010$	$S_4 = 010$	$S_6 = 011$	0	0
$S_5 111$	$S_5 = 111$	$S_4 = 010$	0	0
$S_6 011$	$S_1 = 000$	$S_6 = 011$	0	1

← state assignments included here

$S_7 = 101$ xxx xxx x x

State Diagram

 

Next State Maps

BC \ XA	00	01	11	10
00	1	0	0	0
01	0	x	x	1
11	0	1	0	0
10	0	1	1	0

A⁺

BC \ XA	00	01	11	10
00	1	0	1	1
01	0	x	x	0
11	0	1	1	1
10	1	1	0	1

B⁺

BC \ XA	00	01	11	10
00	0	0	0	0
01	0	x	x	0
11	0	1	0	1
10	0	1	0	1

C⁺

Maps for inputs to flip flops [6]

BC \ XA	00	01	11	10
00	1			
01		x	x	1
11		x		
10		x	x	

Sa

BC \ XA	00	01	11	10
00		1	1	x
01	x	x	x	
11	x		1	x
10	x			x

Ra

← could circle this 1 with the x above.
(alternate answer)

BC \ XA	00	01	11	10
00	1		1	1
01		x	x	
11		x	x	x
10	x	x		x

Sb

BC \ XA	00	01	11	10
00		x		
01	x	x	x	x
11	1			
10		x		

Rb

could circle this 1 with the x below
(alternate answer)

BC \ XA	00	01	11	10
00				
01		x	x	
11		x	x	x
10		1		1

Sc

BC \ XA	00	01	11	10
00	x	x	x	x
01	1	x	x	1
11	1			
10	x		x	

Sc

Output Z

BC \ XA	00	01	11	10
00	1	1		1
01	1	x	x	1
11				1
10		1		

Output Z

alternate answer
 $R_a = A\bar{B} + XAC$

Input/output functions

alternate answer

$$S_b = \bar{A}\bar{C} + XAB$$

$$S_a = \bar{A}\bar{B}\bar{C}\bar{X} + \bar{B}CX$$

$$S_b = \bar{A}\bar{C} + \bar{B}\bar{C}X$$

$$S_c = A\bar{B}X + \bar{A}B\bar{X}$$

$$R_a = A\bar{B} + XB_c$$

$$R_b = \bar{A}C\bar{X} + A\bar{B}\bar{C}X$$

$$R_c = \bar{B} + \bar{A}X$$

$$Z = A\bar{B} + A\bar{B}\bar{X} + \bar{A}CX$$


2. Design a finite state machine as a clocked Mealy sequential network with one input X and one output Z . The machine is a recognizer that has an output trigger sequence and a reset output to zero sequence. If the input sequence '0 1 1 0' occurs then the output changes to '1' coincident with the last bit of the sequence. The output remains at '1' until the reset sequence '0 1 0' is received on the input and, in this case, the output changes to '0' coincident with the last bit of the sequence. Initially, output Z is '0'.

For example,

$X = 0\ 0\ 1\ 0\ 0\ 0\ 1\ 1\ 0\ 0\ 1\ 0\ 1\ 0\ 1\ 1\ 0\ 0\ 0\ 0\ 0\ 1\ 0\ 1$
 $Z = 0\ 0\ 0\ 0\ 0\ 0\ 0\ 0\ 1\ 1\ 1\ 0\ 0\ 0\ 0\ 0\ 1\ 1\ 1\ 1\ 1\ 1\ 0\ 0$


For the design, provide a state graph, the corresponding state table and the output table. Number the states S_0, S_1, \dots . Maximum marks will be given for a correct solution with the minimum number of states. **Do not** continue the design beyond this point. (In particular, there is no need to implement using flip-flops.)

 There are 2 options, depending on whether or not you assume the 0 the ends 0110 can overlap with the 0 that starts 010.



Assuming 0110 and 010

can overlap

 

Assuming 0110 and 010 cannot overlap


State Table and Output Table									
Present	Next		Output		Present	Next		Output	
	$X=0$	$X=1$	$X=0$	$X=1$		$X=0$	$X=1$	$X=0$	$X=1$
S_0	S_1	S_0	0	0	S_0	S_1	S_0	0	0
S_1	S_1	S_2	0	0	S_1	S_1	S_2	0	0
S_2	S_1	S_3	0	0	S_2	S_1	S_3	0	0
S_3	S_4	S_0	1	0	S_3	S_4	S_0	1	0
S_4	S_4	S_5	1	1	S_4	S_5	S_4	1	1
S_5	S_1	S_6	0	1	S_5	S_5	S_6	1	1
S_6	S_4	S_6	1	1	S_6	S_0	S_4	0	1
S_7	S_X	S_X	X	X	S_7	S_X	S_X	X	X

3. Design a four-bit ALU/Register with the functional behaviour described in the table. It has three control inputs **X**, **Y** and **Z** and one 4 bit data input **A(3)**, **A(2)**, **A(1)**, **A(0)** It has one 4 bit data output **D(3)**, **D(2)**, **D(1)**, **D(0)** and one output **O** to indicate arithmetic overflow. Use master slave trailing edge J-K flip-flops for your design.


X	Y	Z	<i>Function</i>
0	0	0	Reset Register to (0000)
0	0	1	Parallel Load from A
0	1	0	Maintain Stored Value
0	1	1	Complement Stored Value
1	0	0	Bit-Wise AND of A and D
1	0	1	Bit-Wise OR of A and D
1	1	0	ADD (A + D)
1	1	1	Set Register to (1111)

Derive a schematic to implement the ALU/Register using J-K, Flip-Flops, Multiplexers, Full-Adders, Inverters, and any other 2-input gates you need. Keep the design as simple as possible.

(see next page)

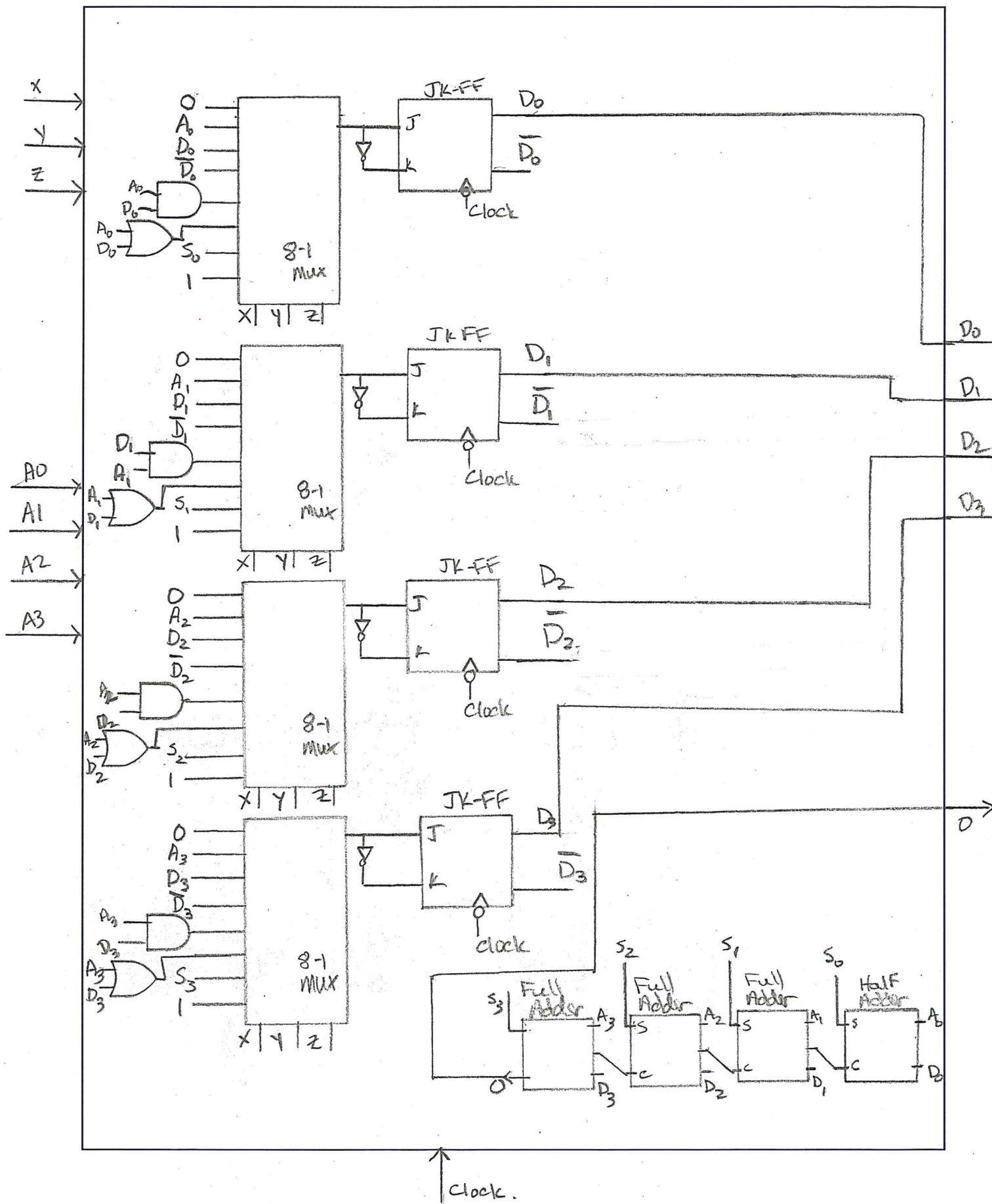

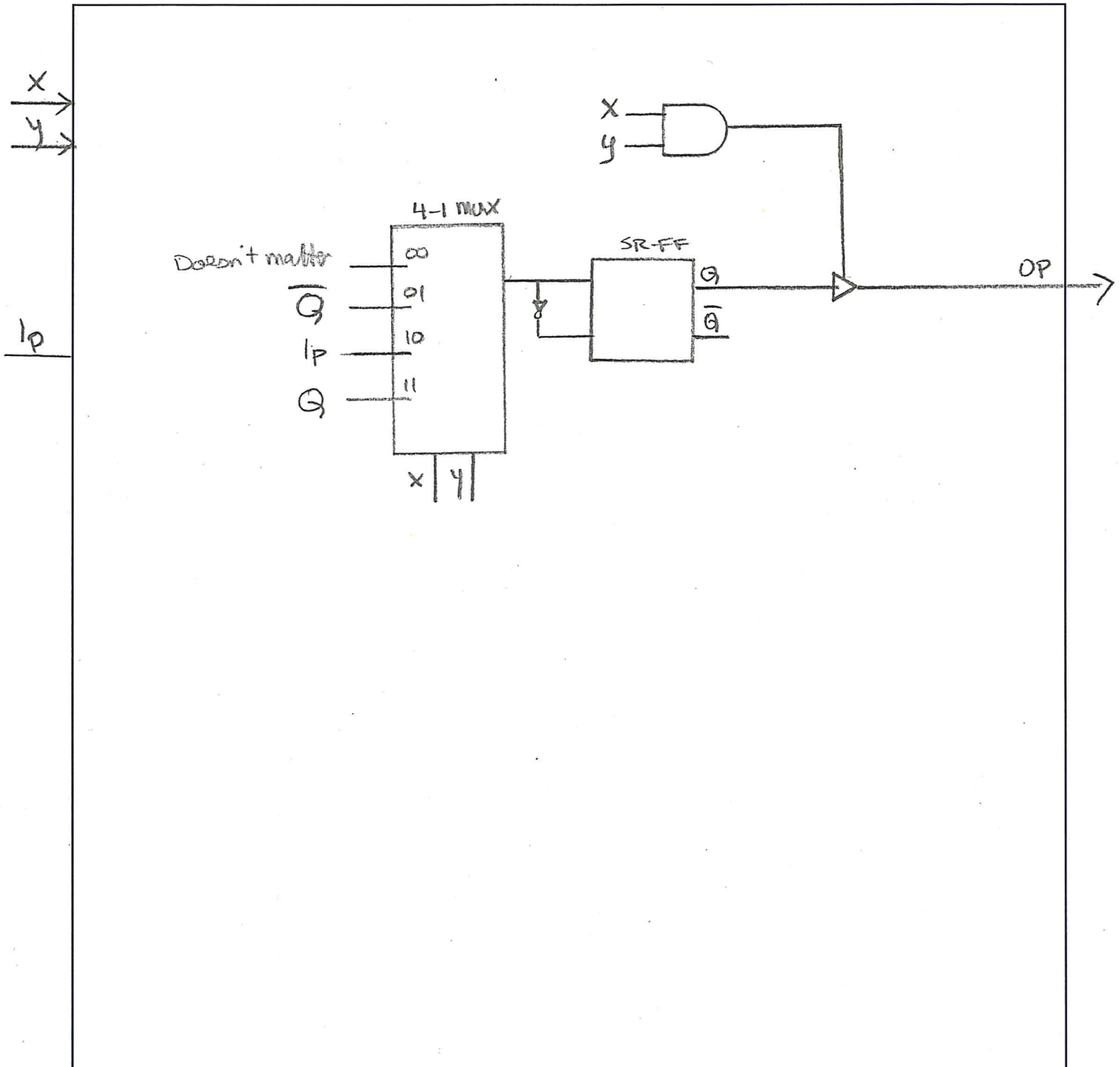4. Design a static RAM memory cell, using a set-reset flip flop for the internal storage and any other devices you require, with the following features. There are two control lines, **X** and **Y**, an input line **Ip**, and an output line **Op** (there is no clock). The values of **X**, **Y** and **Ip** require the following actions to be taken:
- **X** = 0, **Y** = 0 : the memory cell is not selected (flip-flop contents unchanged, **Op** is to be in the high impedance state **Z**)
 - **X** = 1, **Y** = 1 : read the memory cell (output **Op** is equal to contents of flip-flop)
 - **X** = 1, **Y** = 0 : write to the memory cell (flip-flop contents to be equal to value on **Ip**, **Op** is to be in the high impedance state **Z**)
 - **X** = 0, **Y** = 1 : toggle the memory cell (invert the flip-flop contents, **Op** is to be in the high impedance state **Z**).



5. A gated latch (G-L FF) behaves as follows:

- If $G = 0$, the flip-flop does not change state.
- If $G = 1$, the next state of the flip-flop is equal to the value of L , where G and L are the two inputs to the flip flop.

Derive the characteristic (next- state) equation for the flip-flop.


state table


G	L	Q	Q^+
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$G \backslash LQ$	00	01	11	10
0	0	1	1	0
1	0	0	1	1

$$Q^+ = \bar{G}Q + GL$$

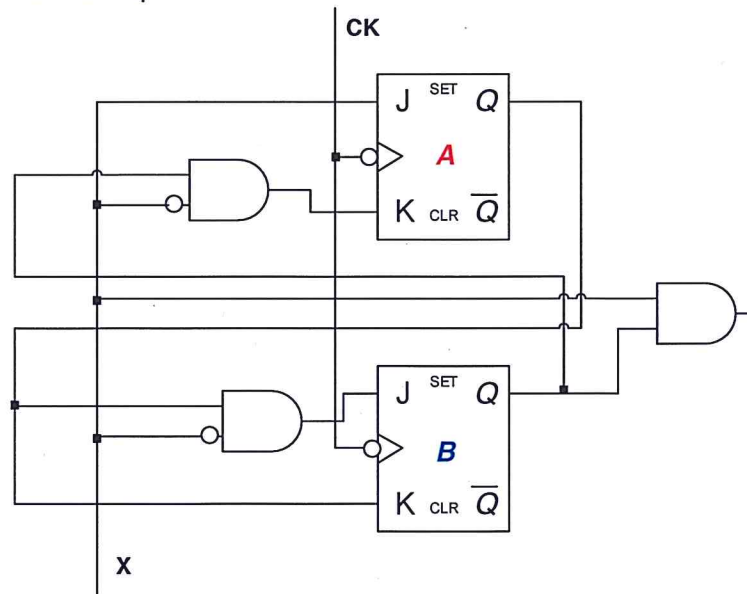6. Complete the timing diagram for the sequential circuit shown.



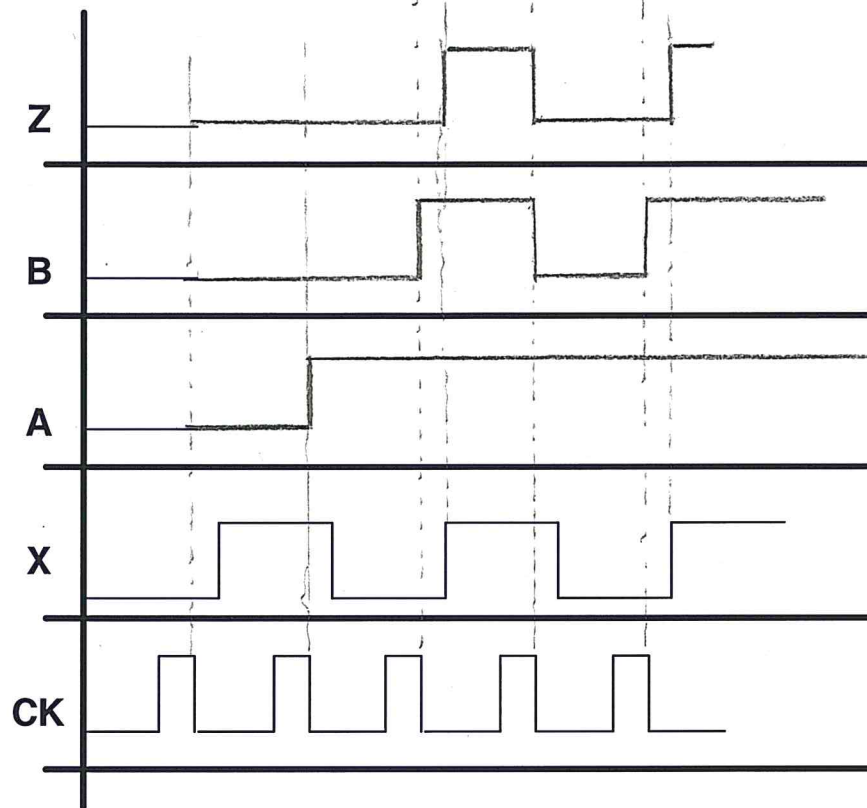

7. 4TH EDITION: Page 442 #8-7. 5th EDITION: Page 432 #7-7 Please inform if 5th edition was used.

Removed

☐ 4th Edition
☐ 5th Edition

8. 4th EDITION: Page 442 #8.8. 5th EDITION: Page 432 #7-8

- a) $\frac{2M}{128K} = \frac{2^{21}}{2^{17}} = 2^4$ BUT the 2M is 8-bit bytes, while the 128K is 2 byte words.
- \therefore #chips needed = $2^4 / 2 = 2^3 = 8$ chips.
- b) $2M = 2^{21}$, so 21 lines are needed to address each byte.
 (see below) 3 lines are addressing each byte, so the remaining 18 connect to all chips.
- c) 8 chips = 2^3 chips \Rightarrow 3 chip select lines.