

**University of Victoria**  
**Department of Computer Science**  
**CSC 355 Digital Logic and Computer Design**  
**ASSIGNMENT 2 DUE Thursday October 14, 2015 AT BEGINNING OF CLASS**

---

Neatness Counts!

It is expected that answers to assignments are either typed or written *\*extremely\** neatly. In all cases, the Karnaugh Maps formats below for *\*must\** be used, either copied and edited to add the required bits and circles or printed and written on. Also, all circuits must be drawn electronically using a circuit drawing package.

---

1. Simplify the following expression, using Boolean algebra, to minimal SOP form. Show (absolutely) every Boolean algebra rule used in the simplification. (Less steps will yield better marks!)

a.  $F_1 = (\bar{A} + B + D)(A + C)(A + \bar{B} + D)(\bar{A} + \bar{C} + \bar{D})(\bar{A} + C)$

$$F_1 = (A' + B + D)(A' + C)(A + B' + D)(A + C)((A' + C' + D')(A' + C)$$

commutative & Idempotent

$$F_1 = [A' + (B + D).C][A + (B' + D).C][A' + (C' + D').C]$$

distributive

$$F_1 = (A' + BC + CD)(A + B'C + CD)(A' + CC' + D'C)$$

distributive

$$F_1 = (A' + BC + CD)(A' + CC' + D'C)(A + B'C + CD)$$

commutative

$$F_1 = [A' + (BC + CD)(CD')] (A + B'C + CD)$$

distributive

$$F_1 = (A' + BCCD' + CCDD') (A + B'C + CD)$$

distributive

$$F_1 = (A' + BCD') (A + B'C + CD)$$

Idempotent & Complement

$$F_1 = AA' + A'B'C + A'CD + ABCD' + BB'CCD' + BCCDD'$$

distributive

$$F_1 = A'B'C + A'CD + ABCD'$$

Complement

b.  $F_2 = \bar{W} \bar{Y} Z + \bar{W} \bar{X} Y + \bar{W} X \bar{Y} + \bar{X} Y \bar{Z}$

$$= \bar{W} \bar{Y} Z + \bar{W} \bar{X} Y(Z + \bar{Z}) + \bar{W} X \bar{Y} + \bar{X} Y \bar{Z}$$

complement, identity

$$= \bar{W} \bar{Y} Z + \bar{W} \bar{X} YZ + \bar{W} X \bar{Y} + \bar{W} \bar{X} Y\bar{Z} + \bar{X} Y \bar{Z}$$

distributive, commutative

$$= \bar{W} Z(\bar{Y} + \bar{X} Y) + \bar{W} X \bar{Y} + \bar{X} Y \bar{Z}$$

absorption, distributive

$$= \bar{W} Z(\bar{Y} + \bar{X}) + \bar{W} X \bar{Y} + \bar{X} Y \bar{Z}$$

simplification

$$= \bar{W}(Z\bar{Y} + Z\bar{X} + X\bar{Y}) + \bar{X} Y \bar{Z}$$

distributive, distributive

$$= \bar{W}(Z\bar{X} + X\bar{Y}) + \bar{X} Y \bar{Z}$$

consensus

$$= \bar{W} \bar{X} Z + \bar{W} X \bar{Y} + \bar{X} Y \bar{Z}$$

distributive

c.  $F_3 = (V + Y + Z)(\bar{V} + W + \bar{X})(\bar{V} + X + \bar{Y})(V + \bar{X})$

$$F_3 = (VV + VX' + VY + VZ + X'Y + X'Z)(V'V' + V'X + V'Y' + V'W + V'X' + XW + Y'W + X'Y')$$

Distributive

$$F_3 = (V + VX' + VY + VZ + X'Y + X'Z)(V' + V'X + V'Y' + V'W + V'X' + XW + Y'W + X'Y')$$

Idempotent

$$F_3 = (V + X'Y + X'Z)(V' + XW + Y'W + X'Y')$$

Absorption

$$F_3 = VXW + VY'W + VX'Y' + V'X'Y + V'X'Z + X'Y'WZ + X'Y'Z$$

Distributive

$$F_3 = VXW + VY'W + VX'Y' + V'X'Y + V'X'Z + X'Y'WZ + X'Y'Z$$

Distributive

$$F_3 = V(XW + Y'W + X'Y') + X'(V'Y + V'Z + Y'Z)$$

Absorption


$$F_3 = V(XW + X'Y') + X'(V'Y + Y'Z)$$

Distributive

$$F_3 = V(XW + X'Y') + X'(V'Y + Y'Z)$$

Consensus

 
2. An *Implication* gate has two inputs (X and Y); the output is 1 except when X=1 and Y=0



Realize the function  $F = \bar{A}B + A\bar{C}$  using only implication gates.


- Note: Only A, B, C and 0 and 1 may be used as gate inputs.
- Hint: 4 gates are sufficient.
 
$$F = A'B + AC' = ((A'B + AC')')' = ((A'B)' \cdot (AC')')' = ((A+B)' \cdot (A'+C))' = (A+B')' + (A'+C)'$$



 3. Find a minimum network to realize  $F = \overline{A} \overline{B} \overline{D} + \overline{B} \overline{C} \overline{D}$  using only 2-input NOR gates. Only A, B, C and D are available and not their complements. (4 gates are sufficient).  
 $F = (A+B+D)' + (C+B+D)'$

$$F = D'(A'B' + B'C') = \overline{D + (A'B' + B'C')} = \overline{D + ((\overline{A+B}) + (\overline{B+C}))}$$



4. Find a *minimum* network to realize  $Z = abe'f + c'e'f + d'e'f + gh$  using only 2-input NAND gates.

- First try to minimize in SOP form:

Note that G and H are only in 1 term, so can't be combined differently.


The remaining terms all contain  $E'F$ , factoring that out, indicates clear minimal result:

$$Z = E'F(AB + C' + D') + GH$$


- Okay, so we need to get everything into 2-input gates:

$$Z = E'(F(AB + C') + FD') + GH$$

- Next make from And & Or gates:

 

- Then convert all to NAND gates:

 


Thus, 8 NAND gates plus 2 interters, or 10 NAND gates.


5. Consider the function specified by the Karnaugh map below:

AB\CD	00	01	11	10
00	1	1		1
01	1	1	1	
11			1	
10			1	

 a. Realize the function using an 8-to-1 multiplexer with control inputs A, C and D.



 b. Repeat, this time realize the function using a 4-to-1 multiplexer. Select the control inputs to minimize the number of added gates.



6. One of:


- Text (Mano, Kime, Martin, 5<sup>th</sup> edition) , page 106 #2-29; or
- Text (Mano, Kime, 4<sup>th</sup> edition) , page 330 #6-4.

Propagation delay of the circuit is on the path with largest number of gates (from D' or C to F).  
 $PD = 0.073 + 0.073 + 0.048 + 0.073 = 0.267$

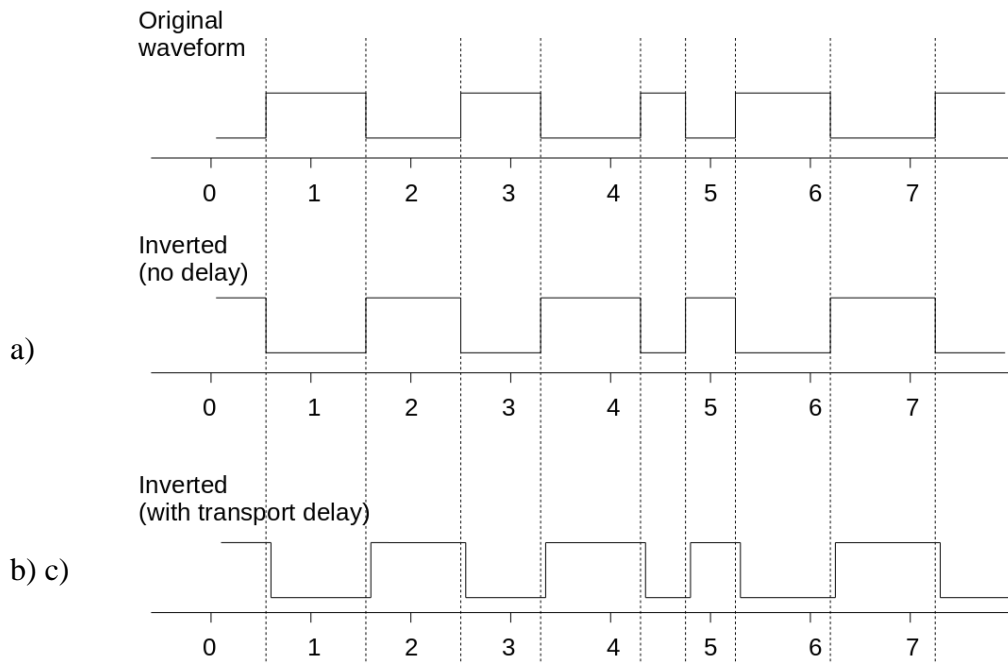7. One of:

- Text (Mano, Kime, Martin, 5<sup>th</sup> edition) , page 107 #2-30; or
- Text (Mano, Kime, 4<sup>th</sup> edition) , page 330 #6-5.

As the rejection time is much smaller than two successive changes in the waveform, the waveform of b) and c) are the same.



8. One of:

- Text (Mano, Kime, Martin, 5<sup>th</sup> edition) , page 107 #2-31; or
- Text (Mano, Kime, 4<sup>th</sup> edition) , page 331 #6-6.

- The longest path, with 4 NAND gates, will have the longest delay. If all gates have output 0 and transition to 1, the longest possible delay would occur. However, we must first analyze to see if it is possible to have all gates in output 0:

A	B	C	D	1	2	3	F	#0's
0	0	0	0	1	0	1	0	2
0	0	0	1	1	0	1	0	2
0	0	1	0	1	0	1	0	2
0	0	1	1	0	1	1	0	1
0	1	0	0	1	1	1	1	0
0	1	0	1	1	1	1	1	0
0	1	1	0	1	1	1	0	1
0	1	1	1	0	1	1	0	1
1	0	0	0	1	0	1	0	2
1	0	0	1	1	0	1	0	2
1	0	1	0	1	0	1	0	1
1	0	1	1	0	1	0	1	2
1	1	0	0	1	1	0	1	1
1	1	0	1	1	1	0	1	1
1	1	1	0	1	1	0	1	1
1	1	1	1	0	1	0	1	2

By brute force (!! ) the longest delay will occur when 2 gates have output 0 and transition to 1, while the other 2 on the longest path have output 1 and transition to 0:

$$T_{pd} = 2 \times T_{PHL} + 2 \times T_{PLH} = 2 \times 0.20 + 2 \times 0.36 = 1.12$$

- We calculate tpd for NAND gates as follows:

$$T_{pd} = \frac{T_{PHL} + T_{PLH}}{2} = \frac{0.20 + 0.36}{2} = 0.28$$


If an input appears more than once at input (e.g. B and B') we consider longer delay as its input to output delay.

Input to on longest path (4 gates) =  $4 \times 0.28 = 1.12$

c) they are the same.

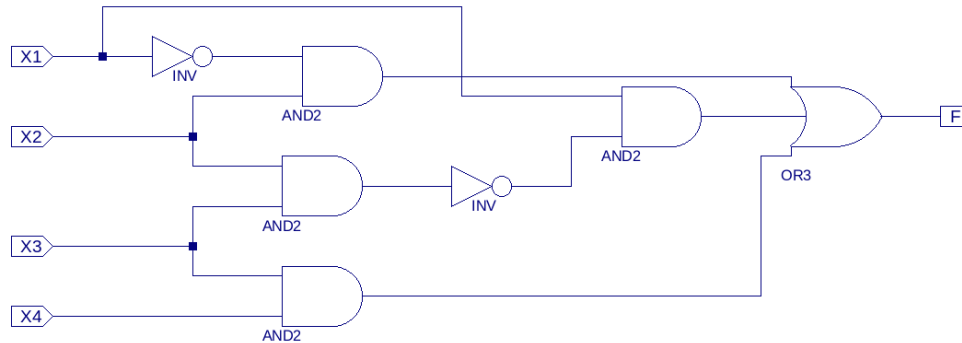9. One of:

- Text (Mano, Kime, Martin, 5<sup>th</sup> edition) , page 109 #2-34
- Text (Mano, Kime, 4<sup>th</sup> edition) , page 201 #4-20



Some Karnaugh maps for your editing pleasure

A\BC	00	01	11	10
0				
1				

AB\CD	00	01	11	10
00				
01				
11				
10				

Change the variables if your expressions require different variable names!

