

**University of Victoria**  
**Department of Computer Science**  
**CSC 355 Digital Logic and Computer Design**  
**ASSIGNMENT 3**

**DUE: Wednesday November 30 IN CLASS**

Neatness Counts!


- Design a finite state machine as a clocked Mealy sequential network with one input **X** and one output **Z**. The machine is a recognizer that has an output trigger sequence and a reset output to zero sequence. If the input sequence '0 1 1 0' occurs then the output changes to '1' coincident with the last bit of the sequence. The output remains at '1' until the reset sequence '0 1 0' is received on the input and, in this case, the output changes to '0' coincident with the last bit of the sequence. Initially, output **Z** is '0'.

For example,

X = 0 0 1 0 0 0 1 1 0 0 1 0 1 0 1 1 0 0 0 0 1 0 1  
 Z = 0 0 0 0 0 0 0 0 0 1 1 1 0 0 0 0 0 1 1 1 1 1 0 0

For the design, provide a state graph, the corresponding state table and the output table. Number the states **S<sub>0</sub>**, **S<sub>1</sub>**, ... Maximum marks will be given for a correct solution with the minimum number of states. **Do not** continue the design beyond this point. (In particular, there is no need to implement using flip-flops.)

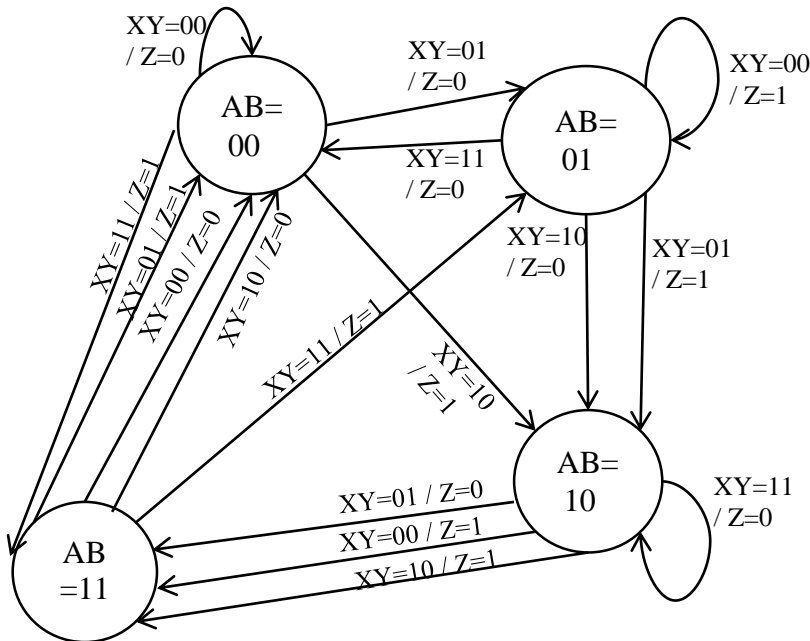- The state diagram for a sequential circuit is given below:



The encoded state table for the circuit is given in Table 5-15 (4<sup>th</sup> edition) or Table 4-14 (5<sup>th</sup> edition) of your textbook.

Assuming the circuit is to be designed using two JK Flip-flops, determine the flip-flop input equations, **J<sub>A</sub>**, **K<sub>A</sub>**, **J<sub>B</sub>**, and **K<sub>B</sub>**.

- Text (Mano, Kime, Martin, 5<sup>th</sup> edition) , page 283 #4-14 – parts a) b) and c) only, or  
 Text (Mano, Kime, 4<sup>th</sup> edition) , page 283 #5-14 – parts a) b) and c) only.


4. A gated latch (G-L FF) behaves as follows:

If  $G = 0$ , the flip-flop does not change state.

If  $G = 1$ , the next state of the flip-flop is equal to the value of  $L$ ,  
where  $G$  and  $L$  are the two inputs to the flip flop.

Derive the characteristic (next- state) equation for the flip-flop.

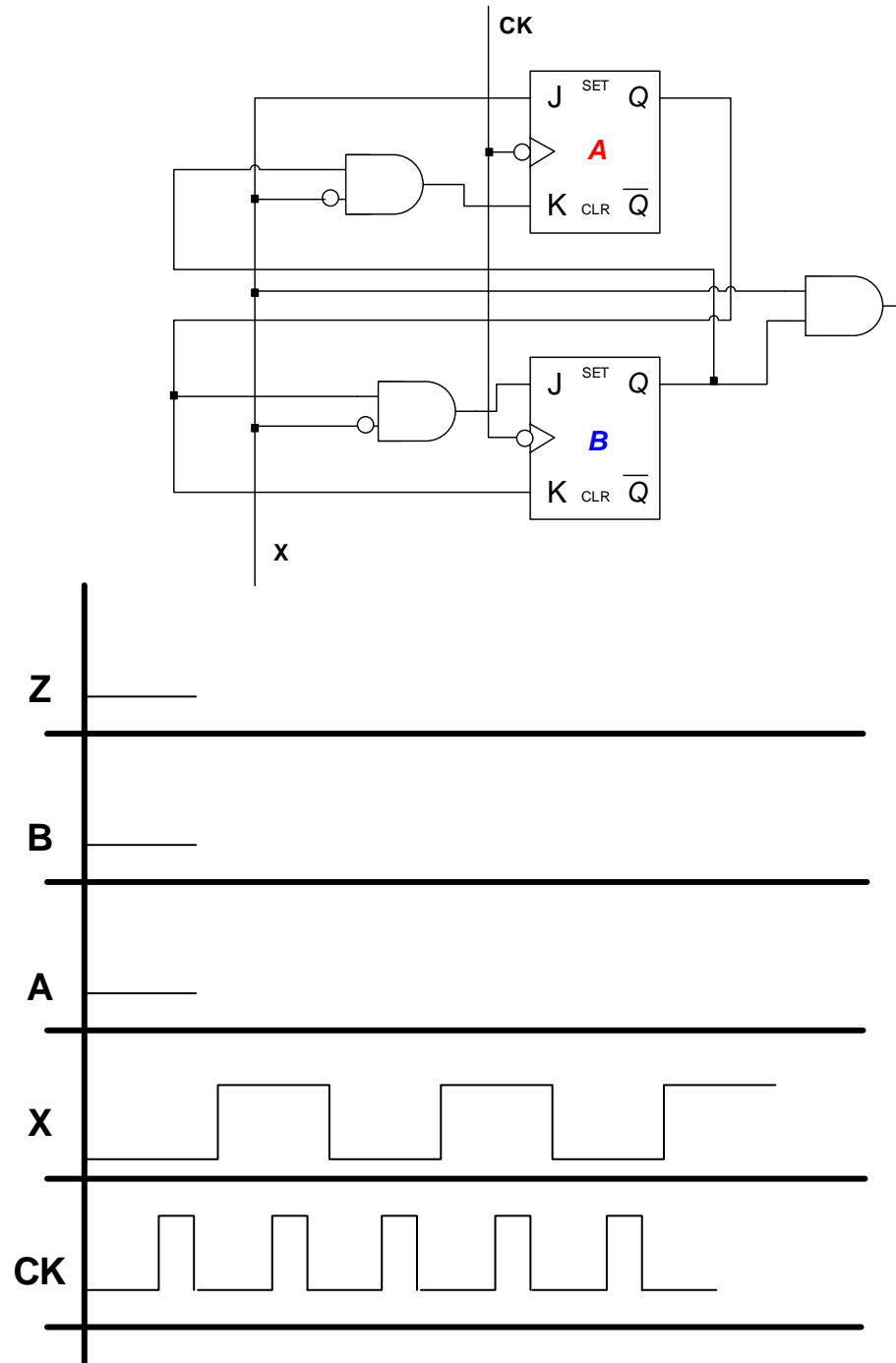5. Complete the timing diagram for the sequential circuit shown.



6. Design a static RAM memory cell, using a set-reset flip flop for the internal storage and any other devices you require, with the following features. There are two control lines, **X** and **Y**, an input line **Ip**, and an output line **Op** (there is no clock). The values of **X**, **Y** and **Ip** require the following actions to be taken:
- **X** = 0, **Y** = 0 : the memory cell is not selected ( flip-flop contents unchanged, **Op** is to be in the high impedance state **Z**)
  - **X** = 1, **Y** = 1 : read the memory cell (output **Op** is equal to contents of flip-flop)
  - **X** = 1, **Y** = 0 : write to the memory cell (flip-flop contents to be equal to value on **Ip**, **Op** is to be in the high impedance state **Z**)
- X** = 0, **Y** = 1 : toggle the memory cell (invert the flip-flop contents, **Op** is to be in the high impedance state **Z**).
7. Text (Mano, Kime, Martin, 5<sup>th</sup> edition) , page 287 #4-23, or  
Text (Mano, Kime, 4<sup>th</sup> edition) , page 287 #5-22.
8. Text (Mano, Kime, Martin, 5<sup>th</sup> edition) , page 287 #4-25, or  
Text (Mano, Kime, 4<sup>th</sup> edition) , page 288 #5-24.
9. Text (Mano, Kime, Martin, 5<sup>th</sup> edition) , page 318 #5-1, or  
Text (Mano, Kime, 4<sup>th</sup> edition) , page 330 #6-1.
10. Text (Mano, Kime, Martin, 5<sup>th</sup> edition) , page 318 #5-2, or  
Text (Mano, Kime, 4<sup>th</sup> edition) , page 330 #6-2.
11. Text (Mano, CANCEL #11 : There is an error in the question number for 4<sup>th</sup> edition!!  
Text (Ma
12. Text (Mano, Kime, Martin, 5<sup>th</sup> edition) , page 478 #8-1  
Text (Mano, Kime, 4<sup>th</sup> edition) , page 490 #9-1
13. Text (Mano, Kime, Martin, 5<sup>th</sup> edition) , page 482 #8-17  
Text (Mano, Kime, 4<sup>th</sup> edition) , page 494 #9-17

Some Karnaugh maps for your editing pleasure

A\BC	00	01	11	10
0				
1				

AB\CD	00	01	11	10
00				
01				
11				
10				

Change the variables if your expressions require different variable names